

Name: _____

Period: _____ Date: _____

Marks: 63 Raw Score: ____ IB Curve: ____

CHAPTER 5 TEST REVIEW


1. The electronvolt is a unit of
 - A. force.
 - B. potential difference.
 - C. energy.
 - D. electric field strength.

(Total 1 mark)

2. Which of the following is a correct unit of electromotive force (emf)?
 - A. $A \Omega^{-1}$
 - B. ΩA^{-1}
 - C. $C J^{-1}$
 - D. $J C^{-1}$

(Total 1 mark)

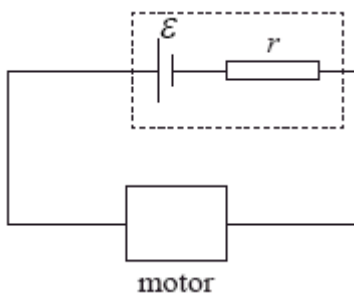3. A cell of emf ϵ and internal resistance r delivers current to a small electric motor.




450 C of charge flows through the motor and 9000 J of energy are converted in the motor. 1800 J are dissipated in the cell. The emf of the cell is

- A. 4.0 V.
- B. 16 V.
- C. 20 V.
- D. 24 V.

(Total 1 mark)

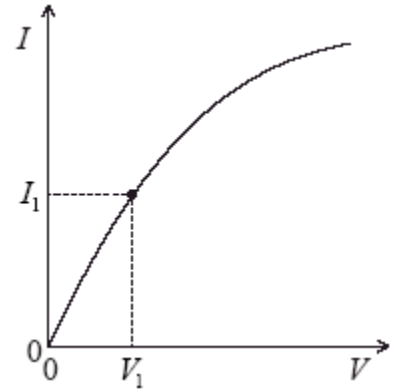4. The graph shows how the current I in a resistor varies with the voltage V applied across it.




Which of the following gives the resistance of the resistor, when $I = I_1$?

- A. $\frac{V_1}{I_1}$
- B. The slope of the curve at the point (V_1, I_1)
- C. $\frac{I_1}{V_1}$
- D. The inverse of the slope of the curve at the point (V_1, I_1)

(Total 1 mark)

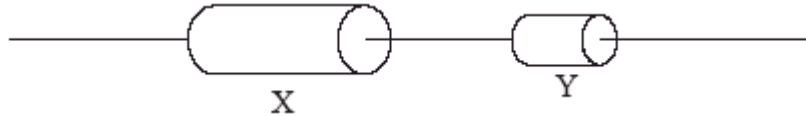5. Two resistors, made of the same material, are connected in series to a battery. The length of resistor X is twice that of resistor Y, and X has twice the cross-sectional area of Y.



Which of the following gives $\frac{\text{resistance of X}}{\text{resistance of Y}}$?

- A. $\frac{1}{4}$
- B. $\frac{1}{2}$
- C. 1
- D. 4



(Total 1 mark)

6. Two rectangular blocks, X and Y, of the same material have different dimensions but the same overall resistance. Which of the following equations is correct?

- A. resistivity of X \times length of X = resistivity of Y \times length of Y
- B. $\frac{\text{length of X}}{\text{cross sectional area of X}} = \frac{\text{length of Y}}{\text{cross sectional area of Y}}$
- C. resistivity of X \times cross sectional area of X = resistivity of Y \times cross sectional area of Y
- D. $\frac{\text{length of X}}{\text{cross sectional area of Y}} = \frac{\text{length of Y}}{\text{cross sectional area of X}}$

(Total 1 mark)

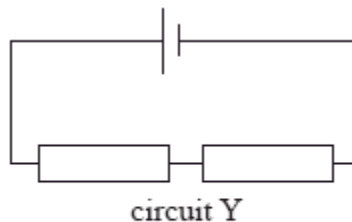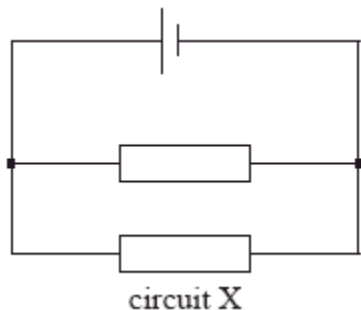7. In the circuits below the cells have the same emf and zero internal resistance. The resistors all have the same resistance.




Which of the following gives the ratio $\frac{\text{power dissipated in X}}{\text{power dissipated in Y}}$?

- A. $\frac{1}{4}$
 B. $\frac{1}{2}$
 C. 2
 D. 4
- (Total 1 mark)

8. In the circuit below, the battery has negligible internal resistance. Three identical lamps L, M and N of constant resistance are connected as shown.

The filament of lamp N breaks. Which of the following shows the subsequent changes to the brightness of lamp L and lamp M?

	Lamp L	Lamp M
A.	stays the same	decreases
B.	increases	stays the same
C.	increases	decreases
D.	decreases	increases

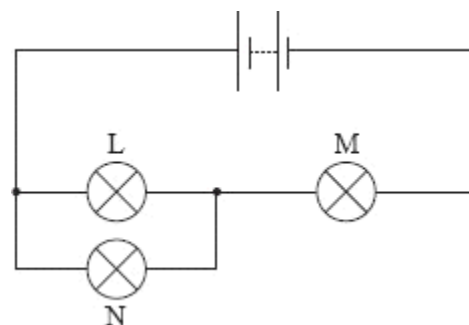


(Total 1 mark)

9. Three identical resistors are connected to a battery as shown.

Which of the following is a correct statement?

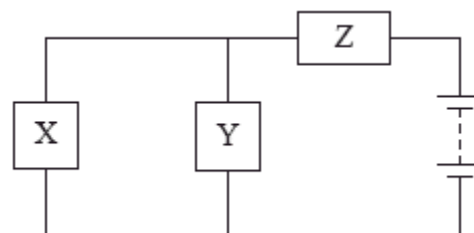- A. The current through X is greater than that through Z.
 B. The potential difference across Z is greater than that across Y.
 C. The potential difference across resistor X and Y together is the same as that across Z.
 D. The current through Z is less than the total current through X and Y.




(Total 1 mark)

10. Two $10\ \Omega$ resistors are connected as shown.

What is the resistance across PQ?

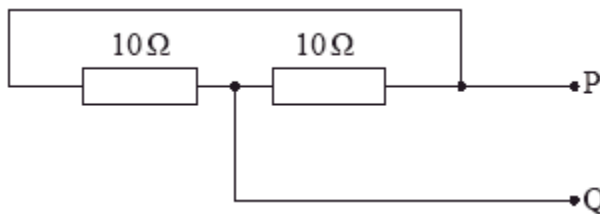- A. $0\ \Omega$
- B. $5\ \Omega$
- C. $10\ \Omega$
- D. $20\ \Omega$




(Total 1 mark)

11. In the circuit shown below, the cell has negligible internal resistance.

Which of the following equations is correct?

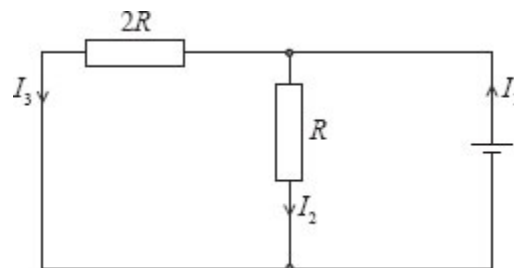- A. $I_1 = 2I_2$
- B. $I_1 = 2I_3$
- C. $I_2 = 2I_3$
- D. $I_3 = 2I_1$




(Total 1 mark)

12. Two $6\ \Omega$ resistors are connected in series with a $6\ \text{V}$ cell. A student **incorrectly** connects an ammeter and a voltmeter as shown below.

The readings on the ammeter and on the voltmeter are

	Ammeter reading / A	Voltmeter reading / V
A.	0.0	0.0
B.	0.0	6.0
C.	1.0	0.0
D.	1.0	6.0

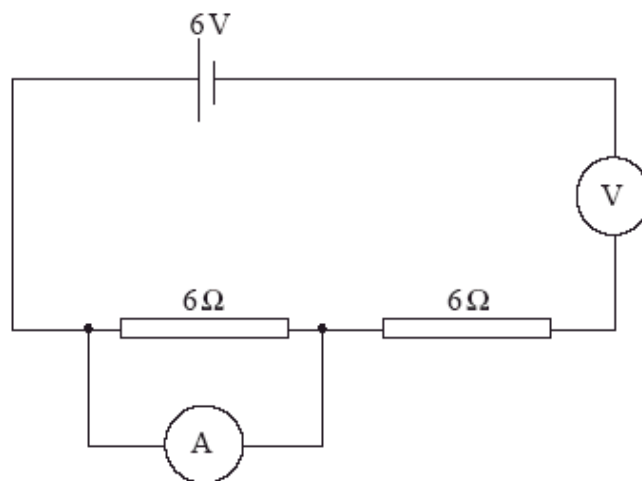


(Total 1 mark)

13. In the circuit below, the voltmeter has a resistance $100\ \text{k}\Omega$. The battery has negligible internal resistance and emf $6\ \text{V}$.

The reading on the voltmeter is

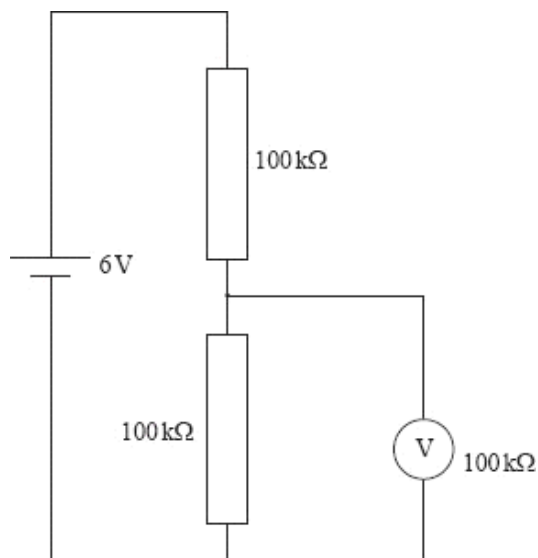- A. $0\ \text{V}$.
- B. $2\ \text{V}$.
- C. $3\ \text{V}$.
- D. $4\ \text{V}$.



(Total 1 mark)

14. This question is about electric charge and resistance.

- (a) A plastic rod XY is held at end X. The end Y is rubbed with a piece of cloth and, as a result, the end Y becomes electrically charged.

The procedure is now repeated using a copper rod and it is found that the copper rod remains electrically neutral. Explain these observations in terms of the properties of conductors and insulators.

.....

.....

.....

.....

.....

.....

.....

.....


.....

.....

.....

(5)

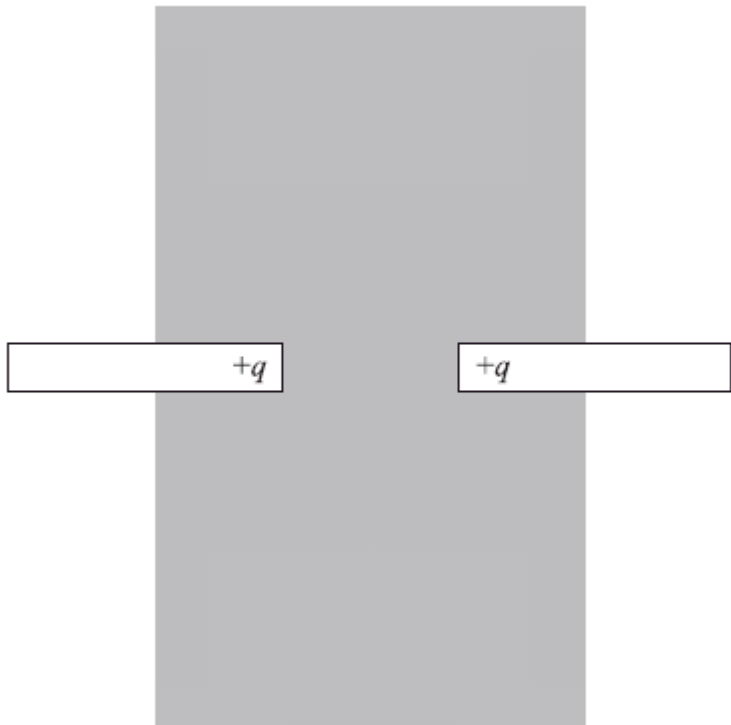- (b) Two plastic rods each have a positive charge $+q$ situated at one end. The rods are arranged as shown.



Assume that the charge at the end of each rod behaves as a point charge. Draw, in the shaded area on the diagram

- (i) the electric field pattern due to the two charges. (2)
- (ii) a line to represent an equipotential surface. Label the line with the letter V. (1)

- (c) A resistor of resistance 1.5Ω is made from copper wire of radius 0.18 mm . The resistivity of copper is $1.7 \times 10^{-8} \Omega \text{ m}$. Determine the length of copper wire used to make the resistor.

.....

(2)

- (d) The manufacturer of the resistor in (c) guarantees that the resistance is within 10 % of 1.5Ω , provided that the power dissipation in the resistor does not exceed 1.0 W .

- (i) Suggest why the resistance of the resistor might be greater than 1.65Ω if the power dissipation in the resistor is greater than 1.0 W .

.....


(2)

- (ii) Show that, for a power dissipation of 1.0 W , the current in a resistor of resistance 1.5Ω is 0.82 A .

.....

(1)

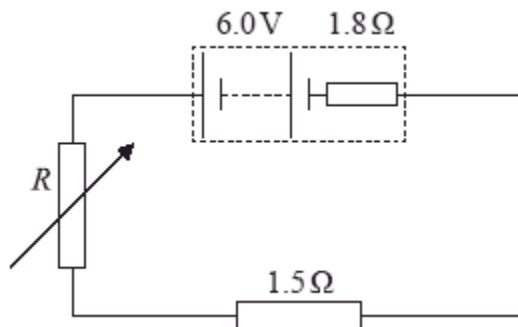- (iii) The 1.5Ω resistor is connected in series with a variable resistor and battery of emf 6.0 V and internal resistance 1.8Ω .



Estimate the resistance R of the variable resistor that will limit the current to 0.82 A .

.....

(3)

15. This question is about electric circuits.

(a) Define

(i) *electromotive force* (emf) of a battery.

.....


(1)

(ii) *electrical resistance* of a conductor.

.....

(1)

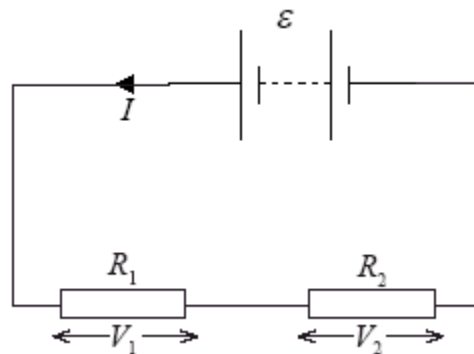(b) A battery of emf ϵ and negligible internal resistance is connected in series to two resistors. The current in the circuit is I .



(i) State an equation giving the total power delivered by the battery.

.....

(1)


(ii) The potential difference across resistor R_1 is V_1 and that across resistor R_2 is V_2 . Using the law of the conservation of energy, deduce the equation below.

$$\epsilon = V_1 + V_2$$


.....

(2)

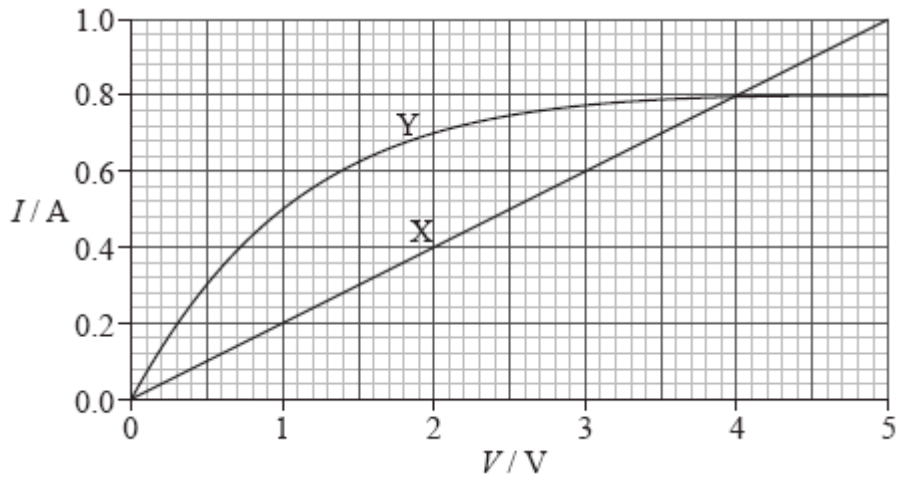(c) The graph shows the I - V characteristics of two conductors, X and Y.




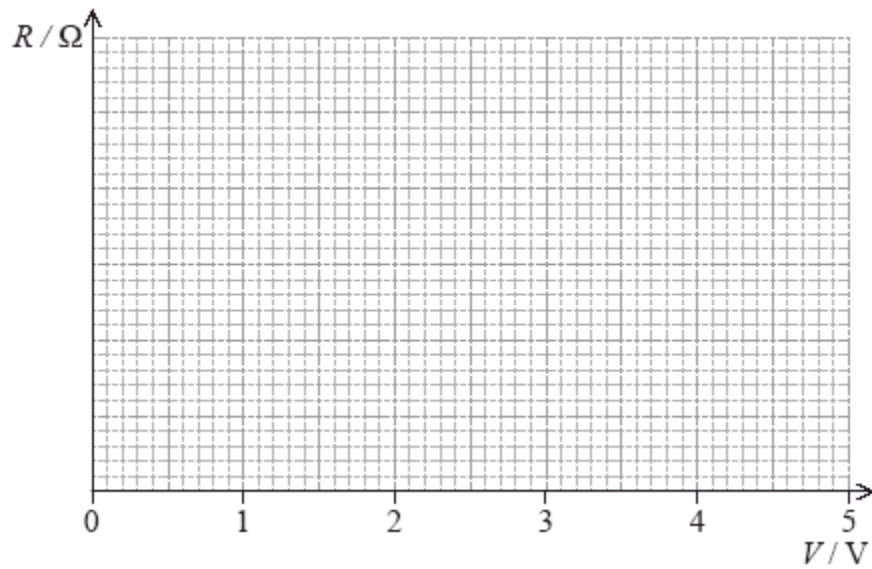On the axes below, sketch graphs to show the variation with potential difference V of the resistance of conductor X (label this graph X) and conductor Y (label this graph Y). You do not need to put any numbers on the vertical axis.



(3)

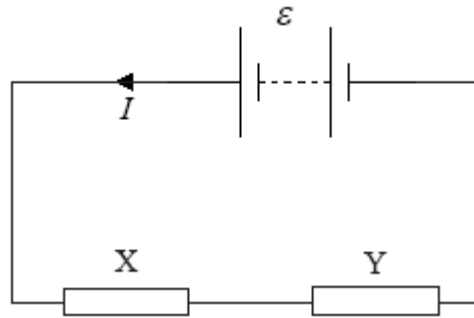- (d) The conductors in (c) are connected in series to a battery of emf ϵ and negligible internal resistance.



The power dissipated in each of the two resistors is the same.

Using the graph given in (c),

- (i) determine the emf of the battery.

.....

(2)


- (ii) calculate the total power dissipated in the circuit.

.....

(2)

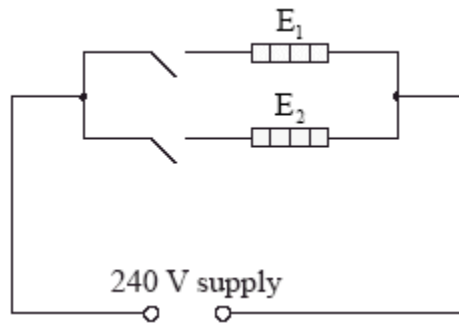16. This question is about an electrical heater.

An electrical heater consists of two heating elements E_1 and E_2 . The elements are connected in parallel. Each element has a switch and is connected to a supply of emf 240 V. The supply has negligible internal resistance.



Element E_1 is made from wire that has a cross-sectional area of $6.8 \times 10^{-8} \text{ m}^2$. The resistivity of the wire at the operating temperature of the element is $1.1 \times 10^{-6} \Omega\text{m}$.

- (a) (i) The total length of wire is 4.5 m. Show that the resistance of E_1 is 73 Ω .

.....

(1)

(ii) Calculate the power output of E_1 with only this element connected to the supply.

.....
.....
.....

(2)

(iii) Element E_2 is made of wire of the same cross-section and material as E_1 . The length of wire used to make E_2 is 1.5 m. Determine the total power output when both E_1 and E_2 are connected to the supply.

.....
.....
.....
.....
.....
.....

(3)

(iv) With reference to the power output, explain why it would be inappropriate to connect the heating elements in series.

.....
.....
.....
.....
.....
.....


(3)

- (b) Each element in the electrical heater is wound as a coil as shown.



Each turn of the coil may be considered to act as a current-carrying long straight wire.

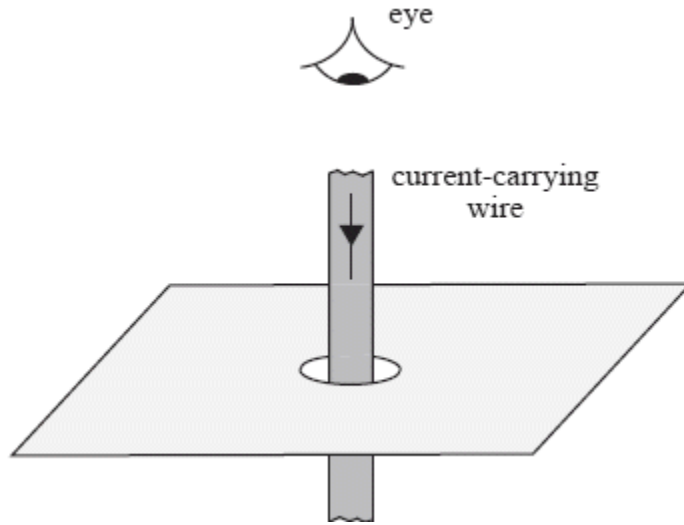- (i) On the diagram, draw the magnetic field around a current-carrying long straight wire. The arrow shows the direction of the current.



(3)

- (ii) State **and** explain whether the turns of wire will attract or repel one another.

.....

.....

.....

.....

.....

(3)

17. This question is about electrical resistance.

- (a) A heating coil is to be made of wire of diameter 3.5×10^{-4} m. The heater is to dissipate 980 W when connected to a 230 V d.c. supply. The material of the wire has resistivity $1.3 \times 10^{-6} \Omega \text{ m}$ at the working temperature of the heater.

- (i) Define *electrical resistance*.

.....

.....

(1)

- (ii) Calculate the resistance of the heating coil at its normal working temperature.

.....

.....

.....



(2)

(iii) Show that the length of wire needed to make the heating coil is approximately 4 m.

.....
.....
.....

(2)

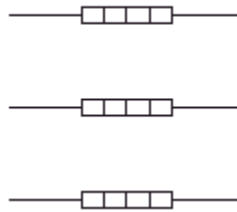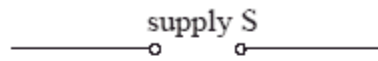(b) Three identical electrical heaters each provide power P when connected separately to a supply S which has zero internal resistance. On the diagram below, complete the circuit by drawing **two** switches so that the power provided by the heaters may be **either P or $2P$ or $3P$** .



(2)