

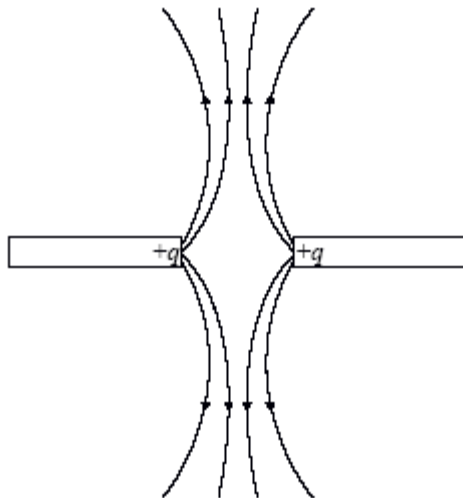

DEVIL PHYSICS
BADDEST CLASS ON CAMPUS

CHAPTER 5 TEST REVIEW -- MARKSCHEME

1. C	4. A	7. D	10. B	13. B
2. D	5. C	8. C	11. C	
3. D	6. B	9. B	12. B	

14. (a) in the plastic there are no free electrons;
 (but) electrons can be transferred to/from the cloth (by friction)
 leaving an imbalance of charge on the rod / *OWTTE*;
 electrons can move freely in copper;
 electrons transferred from/to the cloth from/to the rod;
 because the body is a conductor;
 will flow to/from Earth leaving the rod neutral; 5 max

(b) (i)



- at least four field lines (minimum two per rod) to show overall shape of pattern;
 direction of lines all away from poles; 2
Ignore all working outside region.
Any field lines crossing loses first mark even if accidental.

- (ii) any line labelled V perpendicular to the field lines it traverses; (*judge by eye*) 1
Ignore unlabelled lines as they could be field lines.

- (c) use of $l = \frac{RA}{\rho}$; (*allow if correct substitution seen – watch for use of circumference in place of area*) 2

$$= \left(\frac{1.5 \times \pi \times [1.8]^2 \times 10^{-8}}{1.7 \times 10^{-8}} \right) = 9.0\text{m}$$

- (d) (i) the resistance of a conductor/copper/metal increases with increasing temperature;
 increased power (dissipation) leads to higher temperature in the resistor/ resistor heating up; 2

(ii) $I = \left(\sqrt{\frac{P}{R}} \right) \sqrt{\frac{1.0}{1.5}}$;
 (= 0.82 A) 1

Allow working using 0.82 A to show that power is 1.0086 W,
 in this case final answer must be to 2 sig fig or better.

(iii) total resistance = $[R + 3.3]$;
 $6.0 = 0.82[R + 3.3]$;
 to give $R = 4.0 \Omega$; (allow use of 1.65 Ω leading to 3.9 Ω) 3

or

total resistance in circuit = $\frac{6.0}{0.82} = (7.3 \Omega)$;

internal resistance + fixed resistance = 3.3 Ω ;

to give $R = 4.0 \Omega$;

15. (a) (i) the work done per unit charge in moving a quantity of charge completely around a circuit / the power delivered per unit current / work done per unit charge made available by a source; 1

(ii) the ratio of the voltage (across) to the current in the conductor; 1


(b) (i) emf \times current; 1

(ii) total power is $V_1I + V_2I$;
 equating with EI to get result;

or

total energy delivered by battery is EQ ;
 equate with energy in each resistor $V_1Q + V_2Q$; 2

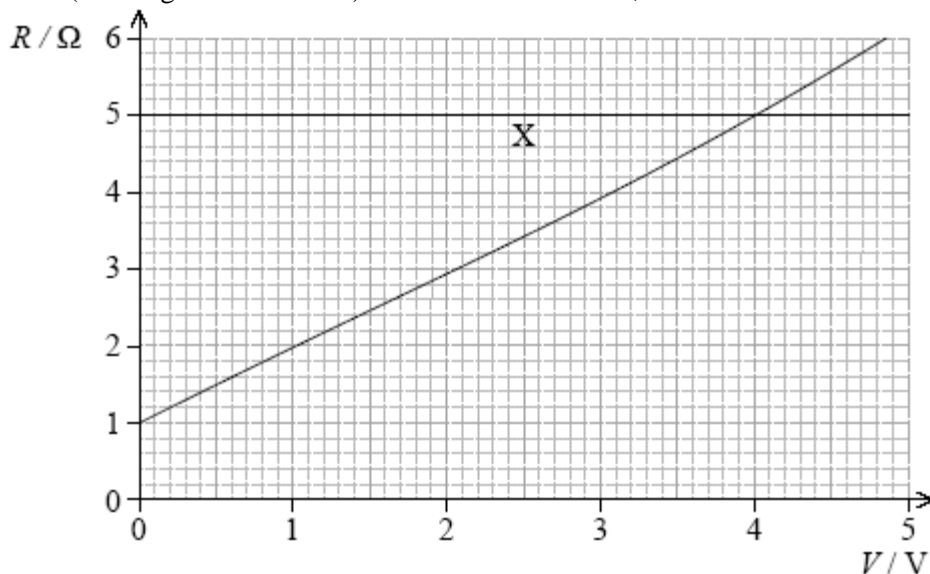(c) graph X: horizontal straight line;
 graph Y: starts lower than graph X;
 rises (as straight line or curve) and intersects at 4.0 V; 3



Do not pay attention to numbers on the vertical axis.

(d) (i) realization that the voltage must be 4.0 V across each resistor;
 and so emf is 8.0 V; 2

- (ii) power in each resistor = 3.2 W;
and so total power is 6.4 W;

or

current is 0.80 A;
so total power is $8.0 \times 0.80 = 6.4$ W;

2

16. (a) (i) use of $R \left(= \frac{\rho l}{A} = \right) \frac{1.1 \times 10^{-6} \times 4.5}{6.8 \times 10^{-8}}$;
72.8 Ω (73 Ω)

1

- (ii) $\frac{240^2}{72.8}$ / shows appropriate alternative equation;
790 W;

2

- (iii) one-third length so E_2 has one-third resistance of E_1 /
evaluates R (24 Ω);
(same V so) $3 \times$ power of E_1 ;
so total power = $4 \times E_1 = 3.2$ kW;

3

or numerical method

current in $R_1 = \frac{728}{240} = 3$ A;

current in $R_2 = 9$ A;

total current = 12 A and total power = 3.2 kW;

Award [3] for correct alternative working.


- (iv) the power output will be less;
because the total resistance is greater in the series case;
hence the current is less and power depends on I^2 ;

$$P = \frac{V^2}{R};$$

3 max

- (b) (i) concentric circles (by eye);
a minimum of three circles required;
correct direction;

3

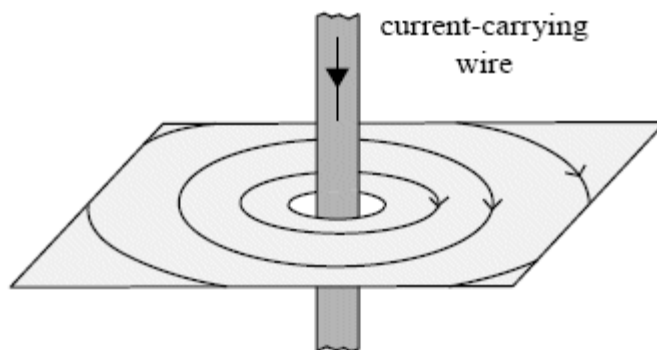

- (ii) current in one turn produces magnetic field in region of adjacent turn;
this gives rise to force in adjacent turn which also has electric current;
they attract;


3

17. (a) (i) ratio of potential difference to current / $\frac{V}{I}$ with terms defined; 1

(ii) resistance = $\frac{230^2}{980}$;
 = 54 Ω ;
 Award [2] for bald correct answer. 2

(iii) $L = \frac{RA}{\rho}$;
 = $\frac{54 \times \pi \times [1.75 \times 10^{-4}]^2}{1.3 \times 10^{-6}}$;
 ($L \approx 4$ m) 2
 Must see re-arrangement of data booklet equation or completely correct substitution as shown in second line for first mark.

(b) e.g.

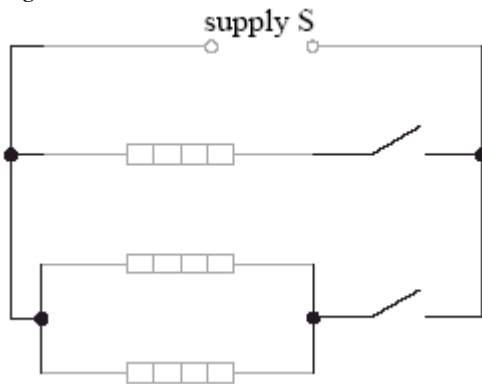

switch connected so that P can be achieved;
 another switch connected so that $2P$ and $3P$ can be achieved;
 Award [0] if three or more switches used. Allow any correct alternative including case where single resistor is permanently connected to supply. There are many variants, this diagram is only one example. 2