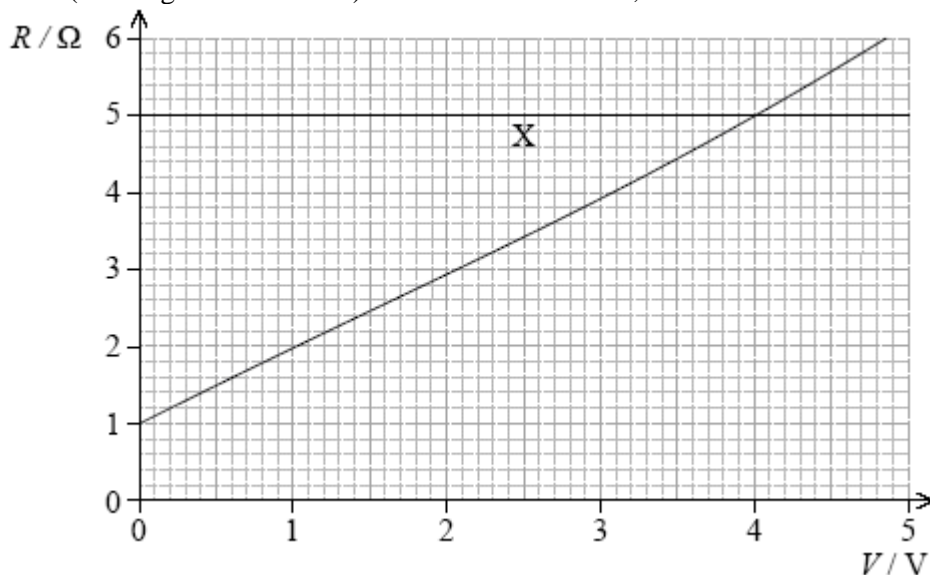


**DEVIL  PHYSICS**  
**BADDEST CLASS ON CAMPUS**

**CHAPTER 5 TEST REVIEW -- MARKSCHEME**

- |      |       |       |       |
|------|-------|-------|-------|
| 1. D | 6. B  | 11. C | 16. A |
| 2. D | 7. C  | 12. C | 17. D |
| 3. C | 8. D  | 13. A | 18. B |
| 4. A | 9. B  | 14. D | 19. D |
| 5. A | 10. C | 15. B |       |

20. (a) (i) the work done per unit charge in moving a quantity of charge completely around a circuit / the power delivered per unit current / work done per unit charge made available by a source; 1
- (ii) the ratio of the voltage (across) to the current in the conductor; 1
- (b) (i)  $\text{emf} \times \text{current}$ ; 1
- (ii) total power is  $V_1I + V_2I$ ;  
 equating with  $EI$  to get result;
- or*
- total energy delivered by battery is  $EQ$ ;  
 equate with energy in each resistor  $V_1Q + V_2Q$ ; 2
- (c) graph X: horizontal straight line;  
 graph Y: starts lower than graph X;  
 rises (as straight line or curve) and intersects at 4.0 V; 3



*Do not pay attention to numbers on the vertical axis.*

- (d) (i) realization that the voltage must be 4.0 V across each resistor;  
 and so emf is 8.0 V; 2
- (ii) power in each resistor = 3.2 W;  
 and so total power is 6.4 W;
- or*
- current is 0.80 A;  
 so total power is  $8.0 \times 0.80 = 6.4$  W; 2

21. (a) use of  $l = \frac{RA}{\rho}$ ; (allow if correct substitution seen – watch for use of circumference in place of area)

$$= \left( \frac{1.5 \times \pi \times [1.8]^2 \times 10^{-8}}{1.7 \times 10^{-8}} \right) = 9.0\text{m}$$

2

(b) (i) the resistance of a conductor/copper/metal increases with increasing temperature;  
increased power (dissipation) leads to higher temperature in the resistor/ resistor heating up;

2

(ii)  $I = \left( \sqrt{\frac{P}{R}} \right) \sqrt{\frac{1.0}{1.5}}$ ;  
(= 0.82 A)

1

Allow working using 0.82 A to show that power is 1.0086 W, in this case final answer must be to 2 sig fig or better.

(iii) total resistance =  $[R + 3.3]$ ;  
 $6.0 = 0.82[R + 3.3]$ ;  
to give  $R = 4.0 \Omega$ ; (allow use of 1.65  $\Omega$  leading to 3.9  $\Omega$ )


3

or


total resistance in circuit =  $\frac{6.0}{0.82} = (7.3 \Omega)$ ;

internal resistance + fixed resistance = 3.3  $\Omega$ ;  
to give  $R = 4.0 \Omega$ ;

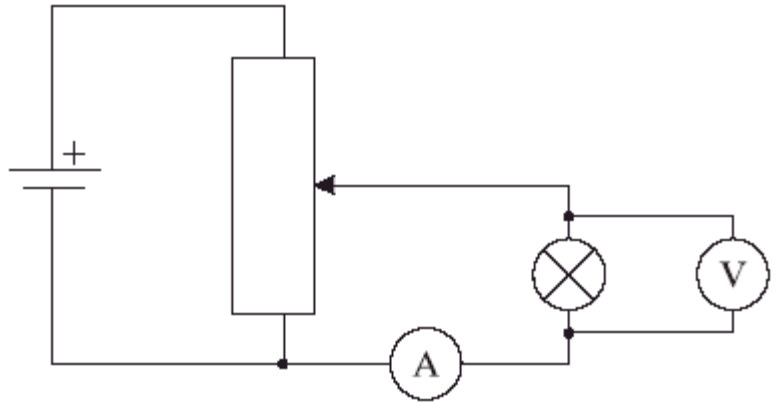22. (a) any circuit in which the current will flow through the lamp;  
variable resistor connected as a potential divider;  
voltmeter across lamp;  
ammeter in series with lamp;



(b) correct shape;  
through origin;

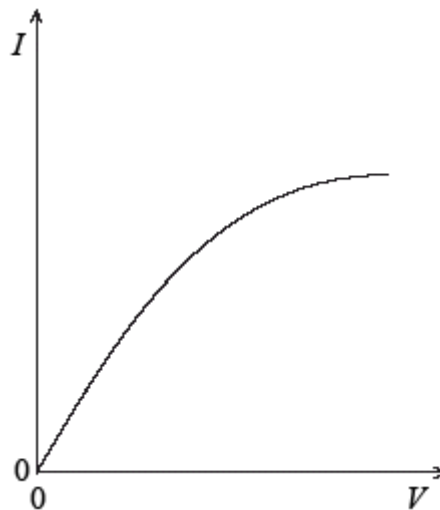


- (c) 0.24 A; 1
- (d) resistance calculated = 5.2(Ω);
- $$A = \left( \frac{\rho l}{R} \right) = 6.2 \times 10^{-8} \text{ m}^2;$$
- radius =  $\sqrt{\frac{A}{\pi}}$  seen/used;
- $$= 1.4 \times 10^{-4} \text{ m};$$
- 4

- (e) calculates resistance of lamps in parallel (2.6 Ω);  
 $V = \varepsilon - Ir$  used to give  $V = 1.0 \text{ V}$ ;  
 1.0 V is lower than 1.25 V / power available to each lamp is 192 mW  
 lower than 300 mW;  
 (terminal pd/power lower) hence not operating normally; *Award [0]*  
*for only stating this bald answer.* 4  
*Watch for ECF from (d).*  
*Award [4 max] for any correct numerical argument involving*  
*energy or power calculations.*

23. (a) there are no positions;  
 the lamp is effectively in series with 100 kΩ no matter what the position of S;  
 this means that the pd across it will always be close to zero (very small) / never  
 reach 6 V;  
*or*  
 the resistance of the filament is much smaller than 100 kΩ;  
 so (nearly) all the potential of the battery appears across the variable resistance; 3  
*Award [0] for incorrect argument or just the answer without any explanation.*

- (b)  $I = \frac{V}{R};$   
 $= \frac{12}{10^5} = 1.2 \times 10^{-4} \text{ A};$

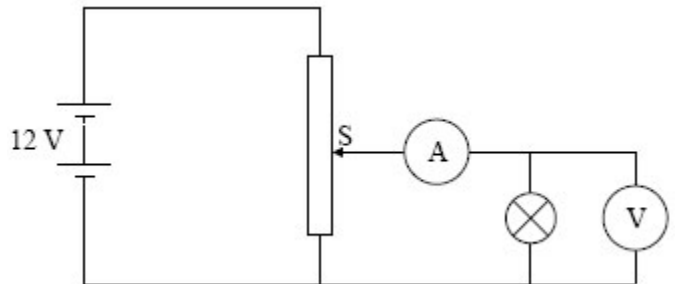- (c) correct position of ammeter;  
 correct position of voltmeter (either to the right  
 or left of the lamp);



24. Domestic shower
- (a) (i) the amount of energy/heat required to raise the temperature of  
 1 kg of a substance through 1K / 1°C; 1
- (ii) energy supplied by heater in 1s =  $7.2 \times 10^3 \text{ J}$ ;  
 energy per second = mass per second  $\times$  sp ht  $\times$  rise in temperature;  
 $7.2 \times 10^3 = \text{mass per second} \times 4.2 \times 10^3 \times 26$ ;  
 to give mass per second = 0.066 kg; 4
- (iii) energy is lost to the surroundings;  
 flow rate is not uniform; 2  
*Do not allow "the heating element is not in contact with all the water*  
*flowing in the unit".*

$$(iv) \quad P=VI \quad I=\frac{P}{V};$$

$$= \frac{7.2 \times 10^3}{240} = 30 \text{ A}; \quad 2$$

(v) when operating at 7.2 kW the element is at a higher temperature/  
 hotter than when first switched on;  
 therefore, resistance is greater (and so current is smaller) / *OWTTE*;  
*or*  
 element is cold / *OWTTE* when first switched on;  
 therefore, smaller resistance than when hot (and so current is larger); 2

$$(b) \quad P = \frac{V^2}{R};$$

$$\frac{240^2}{R_{240}} = \frac{110^2}{R_{110}};$$

$$\frac{R_{110}}{R_{240}} = \left(\frac{110}{240}\right)^2;$$

$$= 0.21$$

*or*

from  $P = VI$

$$240I_2 = 110I_1 \text{ to give } I_2 = \frac{11}{24} I_1;$$

$$I_2^2 R_2 = I_1^2 R_1;$$

$$\frac{R_1}{R_2} = \frac{I_2^2}{I_1^2} = \left(\frac{11}{24}\right)^2;$$

$$= 0.21 \quad 3$$

25. (a) (i)  $v = \sqrt{\frac{2eV}{m}};$

$$v = \sqrt{\frac{2 \times 1.6 \times 10^{-19} \times 250}{9.1 \times 10^{-31}}}$$


$$= 9.4 \times 10^6 \text{ m s}^{-1} \quad 2$$

(ii)  $evB = m \frac{v^2}{r};$

$$r = \frac{9.1 \times 10^{-31} \times 9.4 \times 10^6}{1.6 \times 10^{-19} \times 0.12}$$

$$= 4.5 \times 10^{-4} \text{ m} \quad 2$$

- (b) (i) vector as shown; 1

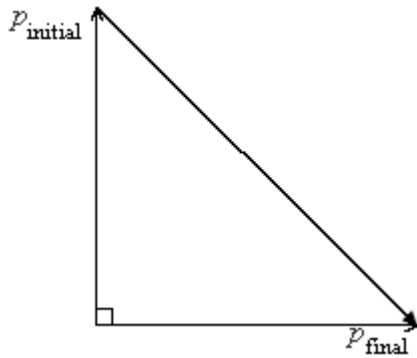

(ii)  $\Delta p = \left( \sqrt{[8.6 \times 10^{-24}]^2 + [8.6 \times 10^{-24}]^2} \right);$   
 $= 1.2 \times 10^{-23} \text{ N s}$  1

(iii)  $F \left( = \frac{\Delta p}{\Delta t} = \frac{1.2 \times 10^{-23}}{7.5 \times 10^{-11}} \right) = 16 \times 10^{-13} \text{ N};$  1