

## Chapter 3

### 3.1 Which statement applies to LEDs?

- A. They can be used with very high currents.
- B. They have a turn-on threshold of about 5V that must be exceeded before current can flow.
- C. They block the flow of electricity in one direction.
- D. They appear brightest when viewed from the side.

### 3.2 Placing resistors in \_\_\_\_\_ increases the total resistance while placing them in \_\_\_\_\_ decreases total resistance.

- A. parallel; series
- B. series; ohm
- C. watt; kirchhoff
- D. series; parallel

### 3.3 Which of these is Ohm's Law?

- A. Current equals Power divided by Resistance.
- B. Current equals Voltage divided by Resistance.
- C. Voltage equals Current divided by Resistance.
- D. All current flowing into a point must flow out of it.

### 3.4 Kirchhoff's Laws are . . .

- A. a basic set of rules for analyzing circuits.
- B. variations of Ohm's Law.
- C. a method of calculating the total resistance of resistors in series and in parallel.
- D. a method of marking resistors with colored bands for easy identification.

### 3.5 Electrical power is . . .

- A. calculated by multiplying the voltage and current together.
- B. a measure of how much energy is moving through a wire.
- C. expressed in Watts.
- D. All of the above.

### 3.6 Which of these statements about resistors is wrong?

- A. Resistors get warm because they convert electrical energy into heat.
- B. They are made from materials like tin and lead.
- C. Resistance is friction between an electric current and the material it is moving through.
- D. Resistors control and limit the flow of electricity.

### 3.7 Copper is a good \_\_\_\_\_ while paper is a good \_\_\_\_\_.

- A. resistor; conductor
- B. insulator; conductor
- C. conductor; insulator
- D. semiconductor; insulator

### 3.8 Nearly all electricity eventually becomes . . .

- A. heat.
- B. information.
- C. garbage.
- D. chemical energy.

### 3.9 Which has the least resistance?


- A. Air.
- B. Distilled water.
- C. Salt water.
- D. Drinking water.

### 3.10 Draw the schematic for a circuit using a battery set, an LED, and two $1\text{K}\Omega$ resistors. The total resistance in the circuit must be less than $1\text{K}\Omega$ , and the LED must light.

### 3.11 Draw the schematic for a circuit using a battery set, an LED, and three $1\text{K}\Omega$ resistors. The total resistance in the circuit must be greater than $2\text{K}\Omega$ , and the LED must light.


### 3.12 Draw the schematic for a circuit using a battery set, an LED, a slide switch, a $100\Omega$ resistor, and a $1\text{K}\Omega$ resistor. The LED must always light and must never have less than $100\Omega$ in series with it. The slide switch should be used to adjust the LED brightness, brighter if the switch is on.

3.13 What will this circuit do?

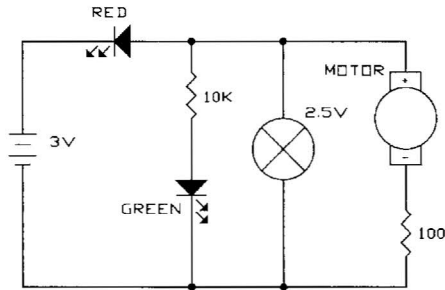


- A. Light the LED.
- B. Light the lamp.
- C. Spin the motor.
- D. Nothing.

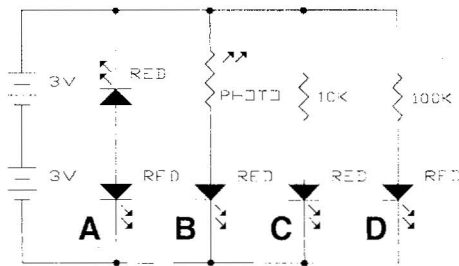3.14 Which LED will be brightest in a dark room?




- A. LED A
- B. LED B
- C. LED C
- D. LED D

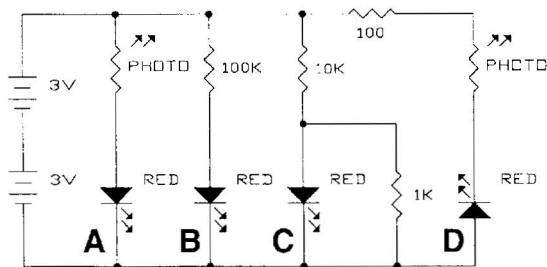3.15 In a bright room which LED will be brightest?




- A. LED A
- B. LED B
- C. LED C
- D. LED D

3.16 What type of logic circuit is this?

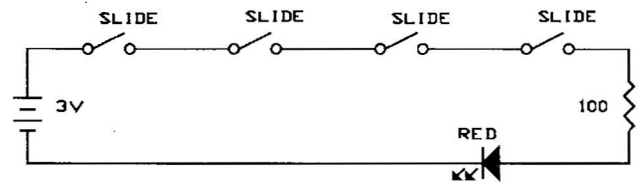

- A. OR
- B. AND
- C. NAND
- D. NOR

3.17 What type of logic circuit is this?

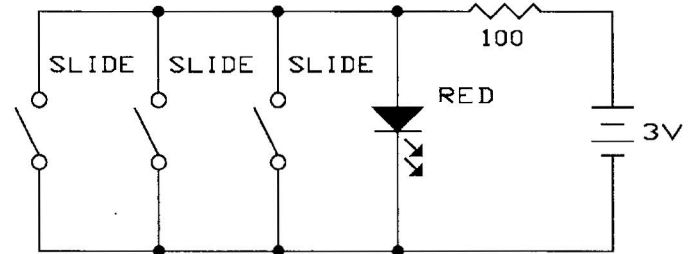

- A. OR
- B. AND
- C. NAND
- D. NOR

3.18 Digital electronics ...

- A. uses computers to process electronic information.
- B. uses a series of numbers to represent an electronic signal.
- C. always gives better performance at lower cost.
- D. always has a display with at least one digit.

3.19 The accuracy of a digital representation of a signal depends on ...

- A. the speed of the microprocessor in the computer.
- B. the voltages used in the measurement.
- C. how accurately and how often the original signal was measured.
- D. the complexity of the circuit.

3.20 Which of these is the name of a circuit that is a basic building block in computers, made up of transistors?

- A. NEVER
- B. ALWAYS
- C. SOMETIMES
- D. AND